



## ARRL Periodicals Archive – Search Results

### A membership benefit of ARRL and the ARRL Technical Information Service

**ARRL Members:** You may print a copy for personal use. Any other use of the information requires permission (see Copyright/Reprint Notice below).

**Need a higher quality reprint or scan?** Some of the scans contained within the periodical archive were produced with older imaging technology. If you require a higher quality reprint or scan, please contact the ARRL Technical Information Service for assistance. Photocopies are \$3 for ARRL members, \$5 for nonmembers. For members, TIS can send the photocopies immediately and include an invoice. Nonmembers must prepay. Details are available at [www.arrl.org/tis](http://www.arrl.org/tis) or email [photocopy@arrl.org](mailto:photocopy@arrl.org).

**QST on CD-ROM:** Annual CD-ROMs are available for recent publication years. For details and ordering information, visit [www.arrl.org/qst](http://www.arrl.org/qst).

**Non-Members:** Get access to the ARRL Periodicals Archive when you join ARRL today at [www.arrl.org/join](http://www.arrl.org/join). For a complete list of membership benefits, visit [www.arrl.org/benefits](http://www.arrl.org/benefits).

### Copyright/Reprint Notice

In general, all ARRL content is copyrighted. ARRL articles, pages, or documents--printed and online--are not in the public domain. Therefore, they may not be freely distributed or copied. Additionally, no part of this document may be copied, sold to third parties, or otherwise commercially exploited without the explicit prior written consent of ARRL. You cannot post this document to a Web site or otherwise distribute it to others through any electronic medium.

For permission to quote or reprint material from ARRL, send a request including the issue date, a description of the material requested, and a description of where you intend to use the reprinted material to the ARRL Editorial & Production Department: [permission@arrl.org](mailto:permission@arrl.org).

**QST Issue:** Jul 1961

**Title:** DX-60 Transmitter Kit

**Author:** George Grammer, W1DF

[Click Here to Report a Problem with this File](#)



## 2009 ARRL Periodicals on CD-ROM

ARRL's popular journals are available on a compact, fully-searchable CD-ROM. Every word and photo published throughout 2009 is included!

- **QST** The official membership journal of ARRL
- **NCJ** National Contest Journal
- **QEX** Forum for Communications Experimenters

**SEARCH** the full text of every article by entering titles, call signs, names—almost any word. **SEE** every word, photo (including color images), drawing and table in technical and general-interest features, columns and product reviews, plus all advertisements. **PRINT** what you see, or copy it into other applications.

**System Requirements:** Microsoft Windows™ and Macintosh systems, using the industry standard Adobe® Acrobat® Reader® software. The Acrobat Reader is a free download at [www.adobe.com](http://www.adobe.com).

### 2009 ARRL Periodicals on CD-ROM

ARRL Order No. 1486  
**Only \$24.95\***

\*plus shipping and handling

Additional sets available:


2008 Ed., ARRL Order No. 9406, \$24.95  
2007 Ed., ARRL Order No. 1204, \$19.95  
2006 Ed., ARRL Order No. 9841, \$19.95  
2005 Ed., ARRL Order No. 9574, \$19.95  
2004 Ed., ARRL Order No. 9396, \$19.95  
2003 Ed., ARRL Order No. 9124, \$19.95  
2002 Ed., ARRL Order No. 8802, \$19.95  
2001 Ed., ARRL Order No. 8632, \$19.95



**ARRL** The national association for **AMATEUR RADIO™**  
SHOP DIRECT or call for a dealer near you.  
ONLINE [WWW.ARRL.ORG/SHOP](http://WWW.ARRL.ORG/SHOP)  
ORDER TOLL-FREE 888/277-5289 (US)

## • Recent Equipment —

### DX-60 Transmitter Kit

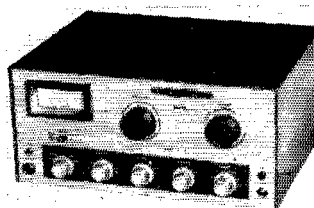

THE Heathkit DX-60 is the third of a series of low-power transmitters that began with the DX-35. The set covers the amateur bands between 3.5 and 30 Mc., has three r.f. stages, and is crystal controlled with provision for operation with an external variable-frequency oscillator. The maximum rated c.w. input of the 6146 final amplifier, 90 watts, can be used on all bands. The 6146 plate tank is a pi network for working into 50- to 75-ohm coaxial line.

On phone the amplifier is screen modulated, with a species of carrier control for squeezing out a bit more power than the plate-dissipation rating of the 6146 otherwise would permit. The audio section of the transmitter uses two dual triodes. One, a 12AX7, is a two-stage speech amplifier. The second is a 6DE7, a tube which has one medium- $\mu$  and one low- $\mu$  triode. The medium- $\mu$  unit is used as a combination speech amplifier and carrier-control tube. The low- $\mu$  section is the modulator, cathode-coupled to the screen of the 6146.

Owners of the DX-40 (the successor to the DX-35) will recognize that the r.f. and the audio tube line-up shown in Fig. 1 is the same as that used in the 40. Interestingly enough, though, the actual r.f. circuit is almost a reversion to the original DX-35 arrangement — that is, the crystal oscillator is an electron-coupled Pierce, and the buffer tank is parallel-tuned. In the DX-40 the oscillator was a Colpitts of the hot-cathode type and a pi network was used to couple the driver to the amplifier.

Several innovations in the DX-60 represent distinct improvements over the earlier models. The 6146 amplifier is now neutralized by the capacitive-bridge method, and the drive-consuming series stabilizing resistor used in the 35 and 40 is no longer needed. There is a potentiometer in the d.c. screen supply to the 6CL6 buffer for controlling grid drive to the 6146; in the

older sets the drive could be controlled only by the tuning of the buffer plate tank. The oscillator and buffer are no longer connected in series across the amplifier plate supply but get their plate and screen power in more orthodox fashion from a 300-volt tap on the plate supply. In the new model, all tubes in the r.f. string are keyed by the grid-blocking method, a separate negative grid-bias supply being incorporated for this purpose. The current in the keyed circuit is only a few milliamperes with this keying system. Finally, there is a built-in low-pass filter between the final tank and the antenna connector for suppressing harmonics in the TV range.

With one exception, the audio setup is the same as in the DX-40, having only minor changes in the circuit constants. The exception is one that builders of the earlier kits will appreciate — there is now an audio gain control in the speech amplifier. True, it's a screwdriver control inside the set and you have to take off the cover to get at it, but at least it's there. In some future model, maybe, it will show up on the panel among the other controls where it can be adjusted as needed.

#### R.F. Circuit

The screen of the 6CL6 oscillator is used as the anode for the Pierce crystal-oscillator circuit. The plate of this tube has a tank circuit permanently tuned to 7 Mc.; this circuit is resonated at around the center of the 7-Mc. range and is not adjustable from the panel. For 7 Mc. and all higher-frequency bands, the following stage, the 6CL6 buffer-multiplier, is driven on 7 Mc. It operates as a straight-through amplifier on 40 meters, as a doubler for 20 meters, as a tripler for 15 meters, and as a quadrupler for 10 meters. Crystals in the 40-meter range are recommended for operation on the last three bands. For 40-meter output either 80- or 40-meter crystals may be used; the crystal oscillator acts as a doubler in the latter

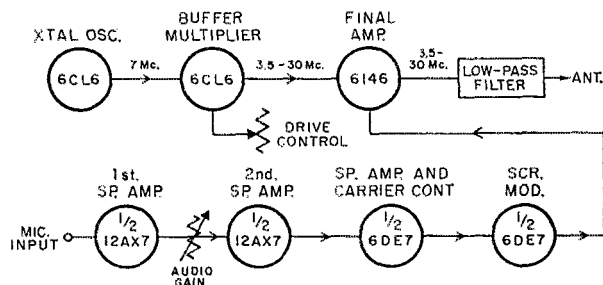



Fig. 1 — Block diagram of the DX-60 transmitter.

case. On 80, there is enough output from an 80-meter crystal to drive the buffer even though the oscillator plate circuit is not tuned to that band. The buffer plate tank uses a sectional coil which is progressively shorted when moving to higher-frequency bands. The band-selector switch is ganged with the band switch in the final plate tank.

The amplifier plate tank similarly has a progressive shorting arrangement for changing the pi-network inductance. The coil is air wound with heavy conductor, and is tuned by a 140- $\mu$ f. variable. On 80 meters an additional 68- $\mu$ f. fixed NP0 ceramic capacitor is shunted across the variable. The output capacitor is a three-section gang with all sections in parallel to give a total capacitance of 1350  $\mu$ f. This capacitor is operated through a 2-to-1 gear reduction so adjustment of loading is not critical on any band. Neither is its tuning excessively slow, as is the case where a small capacitor is shunted by a number of fixed units.

The low-pass filter is a three-section arrangement with *m*-derived end half-sections. The cutoff frequency is 34 Mc. The filter is a much appreciated adjunct to any transmitter, but its presence does mean that the load has to be close to the design value of 50-75 ohms—in other words, coaxial line operating at a low s.w.r.

All three tubes in the r.f. section are biased beyond cutoff in the key-up position. Actual bias is around 130 volts. The key short-circuits part of a voltage divider across the bias supply and completely removes the fixed bias from the oscillator and buffer. With the key down these two tubes are grid-leak biased. Bias for the 6146 final stage is taken from a point a little higher up on the divider and does not disappear completely with the key down; the remaining fixed bias,

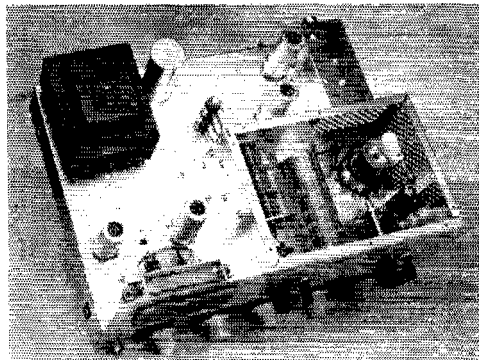

There is no crowding in the DX-60 chassis layout. The 6146 final amplifier and its tank circuit are enclosed in the shield compartment at the right; the perforated cover which completes the shielding has been taken off for this picture. The small enclosure at the rear right edge of the chassis contains the low-pass filter. Tubes alongside it are the 6CL6 oscillator (rear) and 6CL6 buffer-multiplier. The upright resistor at the corner of the amplifier compartment is the power-supply bleeder. Tubes in the left foreground are the 12AX7 speech amplifier and 6DE7 amplifier-modulator.

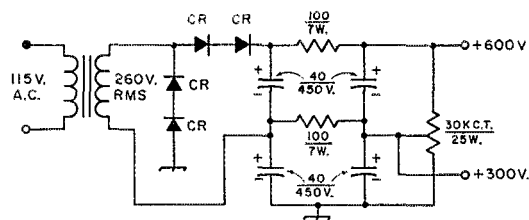


Fig. 2 — The plate power supply in the DX-60 uses a full-wave voltage doubler circuit with silicon rectifiers. Two output voltages are available. The rectifiers, CR, are Sarkes Tarzian Type K, (equivalent to the F-4) having an inverse-peak rating of about 400 volts.

about 25 volts, is enough to protect the tube if through accident it should get no excitation from the buffer-multiplier.


### Keying and Modulation

As is to be expected with keyed oscillators, a small chirp could be detected at the higher frequencies, particularly 10 meters. Most of this was found to be the result of voltage variation on the oscillator screen with keying, and was easily cured by connecting a 150-volt regulator tube between screen and chassis. (There is plenty of room for a 0A2 socket on the chassis near the oscillator tube, in the space between the crystal compartment and the interstage shield.) With this change the keying is quite good through 15 meters and probably won't get criticized even on 10. The activity of the crystal used has something to do with it, of course.

The instruction book does not seem to be as clear as it might be on the question of phone operation. The transmitter is rated at 90 watts peak input, which from our experience with the set means 90 watts peak *envelope* power input. In other words, it will modulate up, on instantaneous voice peaks, to the same input as is used on c.w. This does *not* mean that the plate meter can be kicked up to 150 ma. In the phone position of the function switch the no-modulation plate current is 70 to 80 ma. With full modulation the meter kicks to 90-100 ma. when the p.e.p. input is 90 watts. Any higher plate current causes peak flattening—which, as any phone operator should know, is accompanied by splatter.
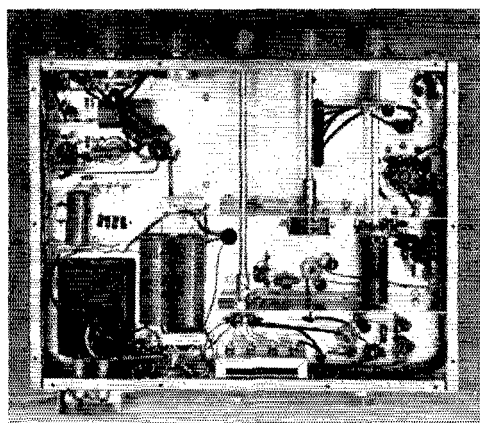
### Power Supply

The 600-volt power supply is of a type that is becoming a favorite with the hi-fi amplifier people—a full-wave voltage-doubling circuit using silicon rectifiers, with an *RC* filter (no chokes). This circuit results in lower peak-inverse voltage across the rectifiers, for the same d.c. output voltage, than is the case with the familiar center-tap rectifier. Thus fewer rectifier units—which are generally rated at 400 volts p.i.v. in the inexpensive types—are needed. With large filter capacitances—the DX-60 has two pairs of 40- $\mu$ f. electrolytics in series, with 100-ohm filtering resistors between—the voltage regulation is good. Key up, the output was measured at 680 volts; key down, 600 volts. The a.c. voltage out



No crowding here, either. Power connections are made through a wiring harness running around three sides of the chassis. Power and bias-supply components occupy the lower left section. The audio circuits are in the upper left corner. Baffle shields separate the below-chassis wiring of the oscillator (lower right), buffer-multiplier, and final amplifier. Crystals plug into the recess at lower center. A.c. is introduced through feedthrough bypasses in the protective cover at lower left. The only departure from the straight kit assembly in this photograph is the "safety" choke connected to the band switch in the upper right corner; none was included in the original circuit diagram.

of the power transformer is a shade over 250 volts r.m.s.

The bias supply uses a half-wave silicon rectifier and *RC* filter working from a separate winding on the power transformer. Heater power for all tubes is taken from the same transformer.

The pilot-light system in the DX-60 was new to this writer, although it may have been used before. The lights are miniature neon bulbs. One is across the bias supply, with a 470K resistor in series to limit the current. This is the POWER ON indicator, since the bias supply is working in all positions of the function switch except OFF. The other bulb is similarly connected across the high-voltage supply. It lights up in the TUNE, AM and CW positions. These lights do not go off immediately when the switch is thrown to an off position,

but stay lit until the filter capacitors are almost discharged — a nice safety feature, although it is a bit startling at first to shut off the power and see the pilots still glowing!

#### Physical

In construction and layout the DX-60 bears practically no resemblance to its forerunners. It has a modern low silhouette, is wider and deeper, and the panel arrangement avoids the monotony of strictly geometrical balance. The chassis and cover (there is no cabinet as such) are of heavy-gauge steel; the cover is the "wrap-around" type with a folded lip that surrounds the top and sides of the panel.

The meter, which reads either grid or plate current of the final stage, has a d'Arsonval movement as compared with the moving-vane type used in the earlier sets, and is well damped. It is recessed and illuminated.

Crystals — there is provision for four — plug into sockets in a recess at the rear of the chassis. It is not necessary to remove a door and reach inside a cabinet to get at them, as it was in the predecessor transmitters.

The transmitter is well shielded and filtered for v.h.f. harmonics. The final amplifier has a complete shield surrounding it, installed on top of the chassis. A bottom plate with plenty of screws is used to box in the circuits under the chassis. A.c. input terminals are brought in through feedthrough capacitors. The low-pass

(Continued on page 144)

#### DX-60 TRANSMITTER

Height: 6 1/4 inches.

Width: 13 3/4 inches.

Depth: 11 1/2 inches.

Weight: 23 pounds.


Power Requirements: 225 watts at 117 volts, 60 cycles.

Price Class: \$85.

Manufacturer: Heath Company, Benton Harbor, Mich.
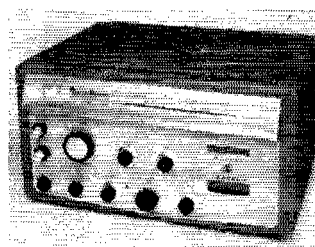
## Viking Invader Transmitter

THE Johnson Viking Invader is a filter-type table-top transmitter capable of operating on all amateur bands between 80 and 10 meters on s.s.b., a.m. and c.w. Power input to the final amplifier, a pair of 6146s, is rated at 200 watts p.e.p. on s.s.b., 200 watts on c.w., and 90 watts on a.m. This can be increased to 2000 watts p.e.p. on



s.s.b., and 1000 watts on c.w. and a.m. by adding an accessory amplifier, the Invader 2000. The high-power linear portion of the Invader 2000 fits inside the Invader's cabinet in place of the power supply, which is removed and remounted on an external power-supply chassis.

The Invader is v.f.o.-controlled and its fre-



## Emblem Decals



Attractive black and gold ARRL emblem decals are available to League members from Headquarters. They measure approximately 4 by 2 inches, will adhere to almost any surface, metal, glass, wood, plastic, and come complete with directions for applying. Use them to dress up your car, station equipment and shack. They're supplied at 10 cents each — no stamps, please — to cover costs.

**AMERICAN RADIO RELAY LEAGUE**  
West Hartford 7, Connecticut

**ART BROWN, W9IHZ,**  
**says, "Let me give**  
**you a quote . . . now!"**



I have the following used gear to trade: (Please use this code to describe it.) 3. Like new, little use; 4. Minor signs of use, no major blemishes; 5. Good condition, with minor modifications; 6. Has major modifications, or requires major repairs

I am interested in purchasing the following new equipment: \_\_\_\_\_

No obligation to buy is implied.

**BROWN electronics inc.**  
**1034 Broadway • Fort Wayne, Indiana**

Name: \_\_\_\_\_

Street No. or R.F.D.: \_\_\_\_\_

City: \_\_\_\_\_

State: \_\_\_\_\_

144

## Recent Equipment

(Continued from page 44)

filter is also completely shielded from the rest of the set.

The transmitter goes together rather easily. Much of the wiring is in a prefabricated harness, and there are no serious mechanical problems in the assembly. An unhurried job of assembly and wiring took us about 15 hours. Two hours were spent inventorying and pretesting components, and another hour sufficed for a postcheck of the wiring against the circuit diagram before actual tryout.

The instruction book does a pretty thorough job of outlining the assembly. One feature that the writer does not recall having seen in earlier Heath books is a double-page spread of drawings identifying all electrical and mechanical parts. The book does seem to be a bit skimpy on circuit description and operating data. We had to figure out from the circuit diagram just what could be expected to happen in each position of the function switch; there was no mention of it in the book. Deciphering those rotary switches with specially-shaped tabs is worse than trying to solve many puzzles!

— G. G.

## Project OSCAR

(Continued from page 63)

as to how these measurements might be made by amateurs.

We also wish to thank Mr. Ed Saxton of Philco Techrep Publications, 1070 East Meadow Circle, Palo Alto, California, for furnishing the computer shown in Fig. 4.

**QST**

## World Above 50 Mc.

(Continued from page 66)

VE3BSZ/V62 were coming into W1-land via aurora along with New York, New Jersey and Pennsylvania stations. Bill also observed a short session on April 25, to W4 area. The above auroral reports both on 50 Mc. The Michigan area is represented by W8PT, Jack, who notes that he heard fourteen states during the aurora of April 14, and that W0MOX, Colorado, was coming through with 5-6 sigs. Jack is active once again on 432 Mc., calling "CQ" at 2215 EST nightly with beam on the Chicago area. To date he has worked W9AAG, W9OH, W9ZIH on 432 Mc., but still needs Michigan. In Chester, Virginia, K4EUS observed a weak aurora on 144 Mc. on April 14, hearing W1LMZ, K2GQI and K2IEJ. Sam (K4EUS) is working on gear for 432 Mc. and expects to be ready to go by the end of May. K9GSC reports several 8s heard and K8JKR in Michigan worked during the auroral session of April 15.

Sideband activity seems to be picking up all over the country on the v.h.f. bands. From W4TLV in Demopolis, Alabama we hear that "I was particularly happy and surprised to hear so many s.s.b. stations on two during the first really good temperature-inversion of the season on April 21, 22, 23. Worked during the three and a half days the band was open, on s.s.b., were: W5AJG, W5FYZ, K5TUP, K5SDM, K5PTG, K5YPI, and W5CTJ. Hearing the tremendous punch of the sideband signals has started a building binge around these parts that should see this station (W4RLV) and W4KCQ on s.s.b. shortly. Rex, W5RCI is

(Please turn the next page)