



ARRL Periodicals Archive – Search Results

A membership benefit of ARRL and the ARRL Technical Information Service

ARRL Members: You may print a copy for personal use. Any other use of the information requires permission (see Copyright/Reprint Notice below).

Need a higher quality reprint or scan? Some of the scans contained within the periodical archive were produced with older imaging technology. If you require a higher quality reprint or scan, please contact the ARRL Technical Information Service for assistance. Photocopies are \$3 for ARRL members, \$5 for nonmembers. For members, TIS can send the photocopies immediately and include an invoice. Nonmembers must prepay. Details are available at www.arrl.org/tis or email photocopy@arrl.org.

QST on CD-ROM: Annual CD-ROMs are available for recent publication years. For details and ordering information, visit www.arrl.org/qst.

Non-Members: Get access to the ARRL Periodicals Archive when you join ARRL today at www.arrl.org/join. For a complete list of membership benefits, visit www.arrl.org/benefits.

Copyright/Reprint Notice

In general, all ARRL content is copyrighted. ARRL articles, pages, or documents--printed and online--are not in the public domain. Therefore, they may not be freely distributed or copied. Additionally, no part of this document may be copied, sold to third parties, or otherwise commercially exploited without the explicit prior written consent of ARRL. You cannot post this document to a Web site or otherwise distribute it to others through any electronic medium.

For permission to quote or reprint material from ARRL, send a request including the issue date, a description of the material requested, and a description of where you intend to use the reprinted material to the ARRL Editorial & Production Department: permission@arrl.org.

QST Issue: Jun 1977

Title: Dual-Band Operation with a 33-Foot Vertical

Author: Wes Hayward, W7ZOI

[Click Here to Report a Problem with this File](#)



2009 ARRL Periodicals on CD-ROM

ARRL's popular journals are available on a compact, fully-searchable CD-ROM. Every word and photo published throughout 2009 is included!

- **QST** The official membership journal of ARRL
- **NCJ** National Contest Journal
- **QEX** Forum for Communications Experimenters

SEARCH the full text of every article by entering titles, call signs, names—almost any word. **SEE** every word, photo (including color images), drawing and table in technical and general-interest features, columns and product reviews, plus all advertisements. **PRINT** what you see, or copy it into other applications.

System Requirements: Microsoft Windows™ and Macintosh systems, using the industry standard Adobe® Acrobat® Reader® software. The Acrobat Reader is a free download at www.adobe.com.

2009 ARRL Periodicals on CD-ROM

ARRL Order No. 1486
Only **\$24.95***

*plus shipping and handling

Additional sets available:

2008 Ed., ARRL Order No. 9406, \$24.95
2007 Ed., ARRL Order No. 1204, \$19.95
2006 Ed., ARRL Order No. 9841, \$19.95
2005 Ed., ARRL Order No. 9574, \$19.95
2004 Ed., ARRL Order No. 9396, \$19.95
2003 Ed., ARRL Order No. 9124, \$19.95
2002 Ed., ARRL Order No. 8802, \$19.95
2001 Ed., ARRL Order No. 8632, \$19.95



ARRL The national association for **AMATEUR RADIO™**

SHOP DIRECT or call for a dealer near you.

ONLINE WWW.ARRL.ORG/SHOP

ORDER TOLL-FREE 888/277-5289 (US)

Hints and Kinks

DUAL-BAND OPERATION WITH A 33-FOOT VERTICAL

One of the more popular antennas for use on the 40-meter band is a quarter-wavelength vertical fed against a suitable radial system. It has long been recognized that this antenna also makes an efficient low-angle radiator for the 20-meter band, offering a gain of a dB or two over a shorter quarter-wave monopole. A typical feed system for two-band operation is shown in Fig. 1. A relay, controlled from the operating position, allows the coax to be connected directly to the antenna for 40-meter operation or through the L-section network for 20-meter operation. The base impedance of the antenna on 20 meters is approximately $1000 + j0$ (see reference 1). The reactance values for the L network are easily calculated by using these data and *Handbook* formulas.

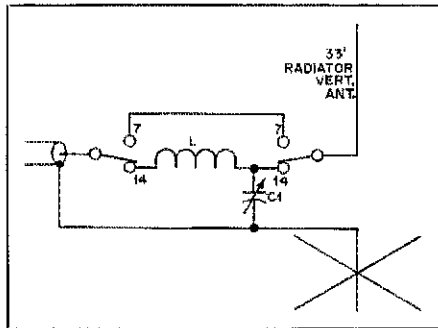


Fig. 1 - Antenna relay for operating antenna on 7 or 14 MHz.

Shown in Fig. 2 is a network that is presently used at the base of the writer's dual-band vertical. The significant departure from the system shown in Fig. 1 is that no relay is required. Operation of the modified network (Fig. 2) is easily understood if it is compared with the simpler L network of Fig. 1. The value of C1, the shunt capacitor, is the same in each network. The reactance of this capacitor at the lower band, 7 MHz, is about 450 ohms. Because this is high when compared with the low base impedance of $35 + j0$ of the antenna, it introduces an insignificant mismatch. The inductor of Fig. 1 has been replaced with a series-tuned circuit. This element has the same net inductive reactance at 14 MHz as does the inductor of Fig. 1. However, the resonant frequency of the series circuit is 7 MHz. Hence, the base impedance of the vertical is unaltered by the L-C2 combination on the 40-meter band.

An iterative approach was used for adjustment of this network. Battery-operated QRP transmitters were used with an rf resistance bridge, allowing all measurements to be done on the roof where the antenna is located. The tap on the inductor was set for near maxi-

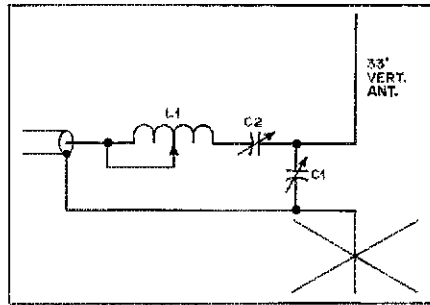


Fig. 2 - Modified L network for dual-band operation.

C1 - 5-80 pF air-variable capacitor.
C2 - 20-300 pF air-variable capacitor.
L1 - 5 mH (maximum) air core.

mum inductance and 7-MHz energy was applied to the bridge. C2 was tuned for minimum VSWR. Then 14-MHz energy was applied and C1 was tuned for minimum VSWR. The match at 14 MHz was poor, initially. The tap on the coil was then moved toward lower inductance. C2 was again adjusted at 7 MHz and C1 was tweaked with 14-MHz excitation. About six iterations of this kind yielded a good match on both bands. The tuning network is housed in a watertight metal box, a requirement of special significance in Oregon. The antenna itself is bolted in a chimney mount with plastic tubing used to insulate the radiator from the mounting brackets. The plastic tubing was the type normally used with golf clubs and is available in most sporting goods stores.

This matching method is undoubtedly not new, although this writer has found no written reference to the application. Using the data for base impedances of vertical radiators presented by Laport (see reference 1), several other cases were studied. The general conclusion reached was that a suitable network could be found to match any practical radiator simultaneously on two bands. It is not necessary that the radiator be resonant on either of the two bands. In the general case the adjustment procedure will not be as straight-forward as that used with the writer's antenna. - *Wes Hayward, W7ZOI*

1) Laport, E. A., *Radio Antenna Engineering*, McGraw-Hill, New York, 1952.

GALVANIC ACTION AND GROUNDS

Whenever two dissimilar metals are in contact, there is a strong possibility of galvanic corrosion. In the presence of moisture a battery is formed, and the more active metal is destroyed. For example, if copper ground radials are connected to a galvanized tower, a copper-zinc battery is formed and the zinc galvanizing is rapidly eaten through.

This process can be stopped by introduc-


ing a "sacrificing anode" of a more active metal such as aluminum. Bury an old chassis or cooking pot after connecting it to one of the tower legs with a short length of wire. The aluminum will corrode instead of the tower.

Periodically, check the condition of the aluminum and the connections. Faulty connections might become a source of TVI. - *Paul Zander, WB6GNN, ex-WA8JCM*

SUNDAY, AND NO WAY TO PADDLE

As I put the finishing touches on my Accu-Keiver on a Sunday afternoon, I was still without the needed paddle. Radio supply stores were closed and there was a lack of money, anyhow. What was the alternative? In desperation, the junk box was raided. All the necessary material to make a paddle was found.

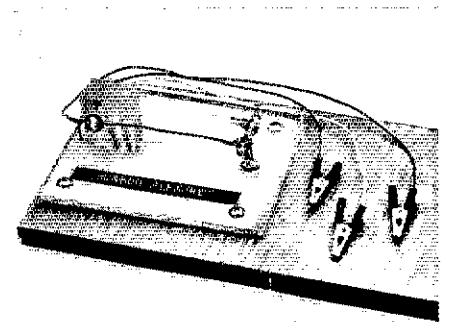The treasures included some Plexiglas from an old storm window. Super Glue became the bonding agent. A plastic ice scraper was used as the base.



The WD8BDQ keyer paddle.

What resulted from my effort was a thing of pleasure. Here is a picture of the original contraption. It is easy to operate and quite satisfactory at most keying speeds. With equipment prices so high these days, it may be worth making a similar unit for your keyer. I was so pleased with mine that I built another (including a case) for use as my permanent keying mechanism. - *Craig V. Iansiti, WD8RDQ*

REMOVING TRANSISTORS FROM PC BOARDS

In order to rapidly remove transistors from pc boards with a minimum amount of damage to the boards, three tools are required. They include a low-heat 20-watt soldering iron, a desoldering bulb, and curved or needle-nosed pliers.

Here is the technique. Place a soldering bridge across two elements of the transistor, using the two closest foils. With the pliers gently pull the transistor while applying the