ADVERTISEMENT



ARRL Periodicals Archive – Search Results A membership benefit of ARRL and the ARRL Technical Information Service

ARRL Members: You may print a copy for personal use. Any other use of the information requires permission (see Copyright/Reprint Notice below).

Need a higher quality reprint or scan? Some of the scans contained within the periodical archive were produced with older imaging technology. If you require a higher quality reprint or scan, please contact the ARRL Technical Information Service for assistance. Photocopies are \$3 for ARRL members, \$5 for nonmembers. For members, TIS can send the photocopies immediately and include an invoice. Nonmembers must prepay. Details are available at www.arrl.org/tis or email photocopy@arrl.org.

QST on CD-ROM: Annual CD-ROMs are available for recent publication years. For details and ordering information, visit www.arrl.org/qst.

Non-Members: Get access to the ARRL Periodicals Archive when you join ARRL today at www.arrl.org/join. For a complete list of membership benefits, visit www.arrl.org/benefits.

Copyright/Reprint Notice

In general, all ARRL content is copyrighted. ARRL articles, pages, or documentsprinted and online--are not in the public domain. Therefore, they may not be freely distributed or copied. Additionally, no part of this document may be copied, sold to third parties, or otherwise commercially exploited without the explicit prior written consent of ARRL. You cannot post this document to a Web site or otherwise distribute it to others through any electronic medium.

For permission to quote or reprint material from ARRL, send a request including the issue date, a description of the material requested, and a description of where you intend to use the reprinted material to the ARRL Editorial & Production Department: permission@arrl.org.

QST Issue: Aug 1971 Title: Ten-Tec Model RX 10 Communication Receiver Author: W4WFL/1

Click Here to Report a Problem with this File



2009 ARRL Periodicals on CD-ROM

ARRL's popular journals are available on a compact, fullysearchable CD-ROM. Every word and photo published throughout 2009 is included!

- QST The official membership journal of ARRL
- NCJ National Contest Journal
- QEX Forum for Communications Experimenters

SEARCH the full text of every article by entering titles, call signs, names—almost any word. SEE every word, photo (including color images), drawing and table in technical and general-interest features, columns and product reviews, plus all advertisements. PRINT what you see, or copy it into other applications.

System Requirements: Microsoft Windows™ and Macintosh systems, using the industry standard Adobe® Acrobat® Reader® software. The Acrobat Reader is a free download at www.adobe.com.

2009 ARRL Periodicals on CD-ROM

ARRL Order No. 1486 Only **\$24.95***

*plus shipping and handling

Additional sets available: 2008 Ed., ARRL Order No. 9406, \$24.95 2007 Ed., ARRL Order No. 1204, \$19.95 2006 Ed., ARRL Order No. 9841, \$19.95 2005 Ed., ARRL Order No. 9574, \$19.95 2004 Ed., ARRL Order No. 9396, \$19.95 2003 Ed., ARRL Order No. 9124, \$19.95 2002 Ed., ARRL Order No. 8802, \$19.95 2001 Ed., ARRL Order No. 8632, \$19.95






Ten-Tec Model RX 10 Communication Receiver

THE RX-10 solid-state receiver is an interesting and attractive addition to Ten-Tec's growing line of practical and inexpensive equipment for amateurs.

Utilizing the synchrodyne direct-conversion circuit, the RX-10 is a "hot" performer on the 80-, 40-, 20-, and 15-meter bands. Selectivity is determined by an audio filter between the mixer and the first audio amplifier. With the 2-kHz bandwidth provided by the filter, ssb reception is excellent. Measured drift is well within the manufacturer's claim of 100 Hz (no warm-up), and, after 30 minutes, ssb signals stay "locked-in." Although single-signal cw reception is not possible with the RX-10, all one has to do to attenuate an interfering signal is to tune to the opposite side of zero beat. Exalted-carrier reception of a-m signals is possible by zero beating the incoming carrier.

The solid-state direct-conversion circuit produces excellent results with a minimum number of components. An incoming signal is heterodyned in the mixer stage with the output of the VFO to produce an audio beat note that is fed through the 2-kHz-wide filter and then to four stages of audio amplification. The output is sufficient to provide comfortable listening, using headphones, on all but the weakest signals.

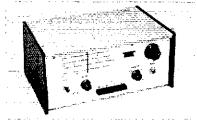

A different approach is used for the oscillator circuit in order to cover four bands. Fig. 1 shows the complete circuit of the oscillator and multiplier stages. Basically, the VFO tunes 3.5 to 4 MHz. When going to 40 meters, L5 is switched into the circuit along with changing the connection for C35, the MAIN TUNE capacitor. C35 is moved over to be in parallel with C40, providing the correct bandspread for 40 meters. The output from the oscillator is amplified in Q8 and then fed to gate 2 of Q1. When going to 14 or 21 MHz, Q9 operates as a multiplier, to provide injection voltage for the detector.

With only 20 feet of wire out a window for an antenna, this writer found the receiver's sensitivity to be impressive on all bands. Care should be taken in the adjustment of the ANTENNA TUNE control to prevent interference from out-of-band stations. This type of interference is caused by envelope detection of very strong signals by the mixer. QRM of this sort can be easily recognized, as it is not affected by the MAIN TUNING. If additional rf selectivity is required, a Transmatch such as the Ten-Tec AC5 should be used.

__ .. _-

OST for


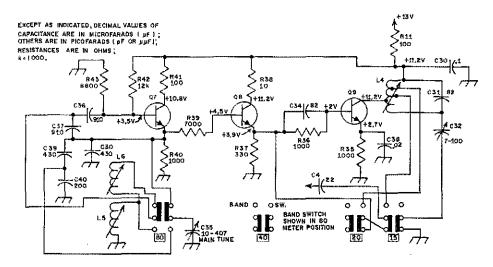


Fig. 1 - This is the circuit of the oscillator and multiplier. All component designations are the same as used in the manufacturer's instruction manual.

An added bonus of special interest to the Novice is the built-in code practice oscillator, which can also be used as a keying monitor. The RX-10 is attractively packaged in a heavy-gauge aluminum cabinet with wood-grained plastic end plates, making a sturdy portable unit. With the option of 117-volt ac or 12-volt dc operation, it should be popular with campers, vacationers, and beginners looking for an inexpensive receiver that will deliver good performance. W4WFL/1

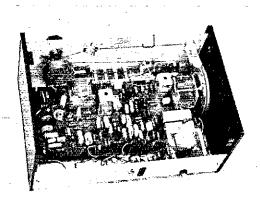Ten-Tec RX-10 Communications Receiver Height: 4 1/2 inches. Width: 10 3/8 inches. Depth: 7 1/4 inches. Weight: 2 1/4 pounds. Power Requirements: 117 volts ac, 50-60 Hz, 1/8 A, or 12 V dc, 35 mA. Price Class: \$60. Manufacturer: Ten-Tec, Inc., Sevierville, TN 37862.



Here's an inside view of the RX-10. The weighted knob on the front panel is used to drive the MAIN TUNING capacitor. The variable capacitor just below the weight knob is the PRESELECTOR tuning.

QST

Regency Electronics HR-2

OST -

- QST -

FM Transceiver

I MAGINE, 1F YOU CAN, a neat looking package measuring $8 \ge 5 1/2 \ge 2 1/4$ inches, into which is carefully packed a double-conversion receiver, and a transmitter with an output power of 10 watts or more. Next, envision some 24 transistors, 2 integrated circuits and 7 diodes, plus all of the other components needed to make up the transceiver. Dream stuff, you say? Not at all! The foregoing description is a word picture of the Regency HR-2 amateur fm station.

The equipment comes with crystals for 146.34/146.94-MHz operation. The company also provides the buyer with a dc power cable, microphone, mobile mounting bracket, and 12 spare crystal sockets which will be discussed later. The rig can be tucked away under the instrument panel of any automobile – large or small – and will still allow ample leg room for all but the most rotund of passengers.

The writer's HR-2 has been in service for some 6 months. It has seen daily use in a 1970 VW car, and despite the rather minuscule battery dimensions there have been no signs of charge depletion even though "somebody" carelessly left the HR-2 power switch in the ON position overnight on a few occasions. (Making a similar mistake with a tube-type mobile unit will normally leave the red-faced operator with a battery whose best effort will provide a mere grunt from the starter when it is engaged.) Solid-state mobile gear, therefore, has its advantages!

Regency rates the transmitter output power at 10 watts. Checks with a calibrated vhf wattmeter showed 13 watts output into a 5/8-wave antenna tuned for an SWR of 1. Operating voltage (engine running) was 13.6 during the tests. Despite Connecticut's rough terrain (small mountains, if you will), the author has never experienced difficulty in working through area repeaters at distances up to 50 or 60 miles. It is worth mentioning, however, that the 5/8-wave antenna contributes significantly to the aforementioned good results. The slight gain over a 1/4-wave whip (approximately 3 dB) can be beneficial under marginal signal conditions.

The only failure experienced to date, and one that appears to be case history with many HR-2 units, was a faulty set of relay contacts. After several hours of use the B+ transfer contacts of the changeover relay apparently become pitted in the transmit position. When this happens it may take numerous squeezes of the mike button to get into the transmit mode. Being unable to obtain a reply from Regency regarding a solution to the problem, owing, perhaps, to faulty mail service, the writer

August 1971

45